
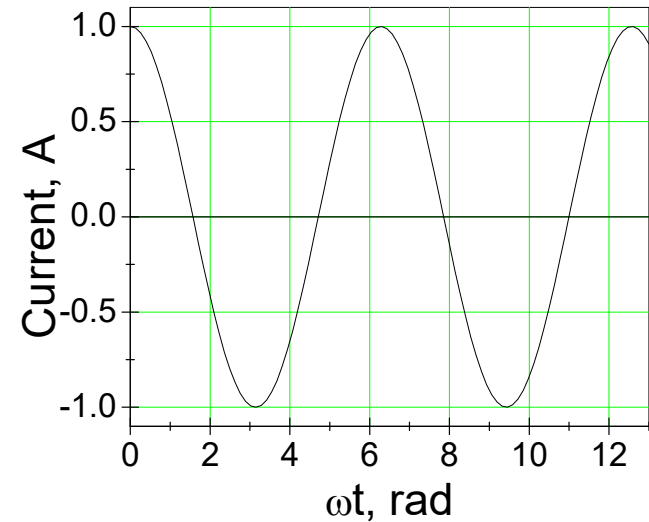


AC power through resistor

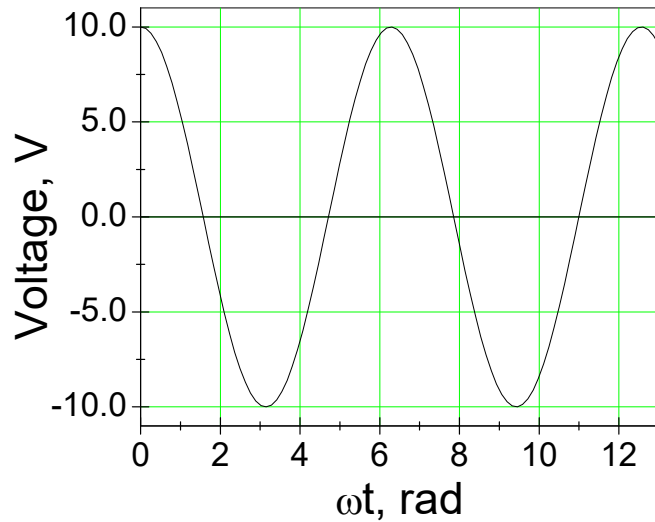Example: $i = I_M \cos(\omega t)$; $I_M = 1 \text{ A}$; $R = 10 \ \Omega \Rightarrow v = V_M \cos(\omega t)$; $V_M = I_M * R = 10 \text{ V}$




The power dissipated in the resistor:

At any point of time, $p(t) = v(t) \times i(t) =$



$$V_M \cos(\omega t) \times I_M \cos(\omega t) = V_M I_M \cos^2(\omega t)$$

$p(t)$ is always positive

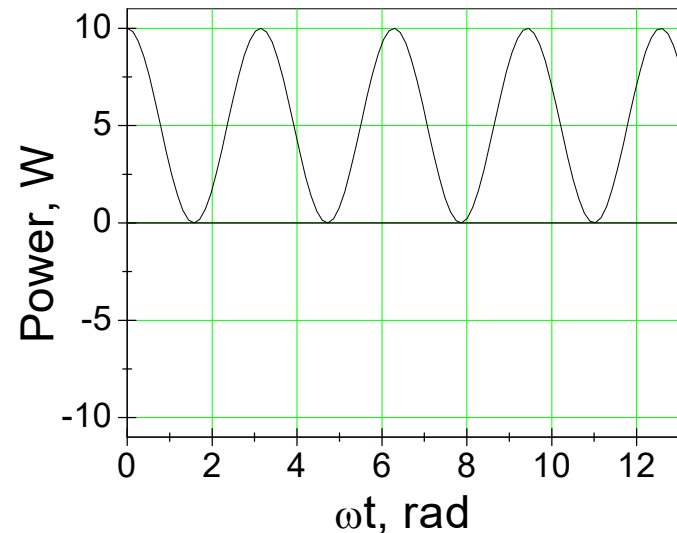

Instantaneous and Average (“rms”) powers

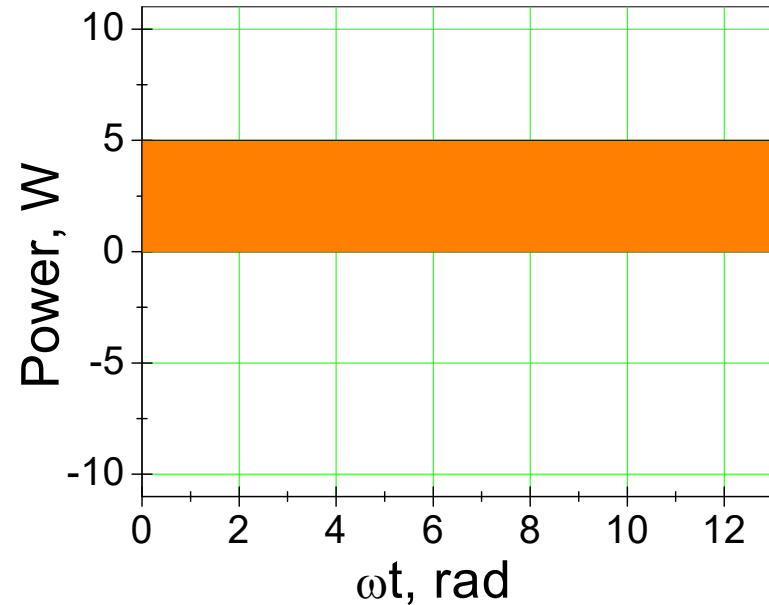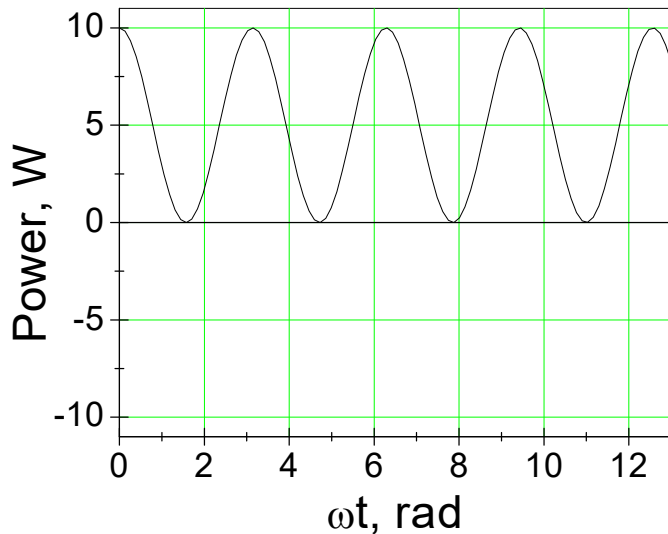RMS = “root mean square” or the square root of the arithmetic mean (average)





Instantaneous power:

$$p(t) = v(t) \times i(t) = V_M I_M \cos^2(\omega t)$$

In terms of *Joule heat dissipation*, instantaneous power is *equivalent* to a certain DC power (i.e. *time-independent*).

The equivalent DC power is called Average or “rms” power

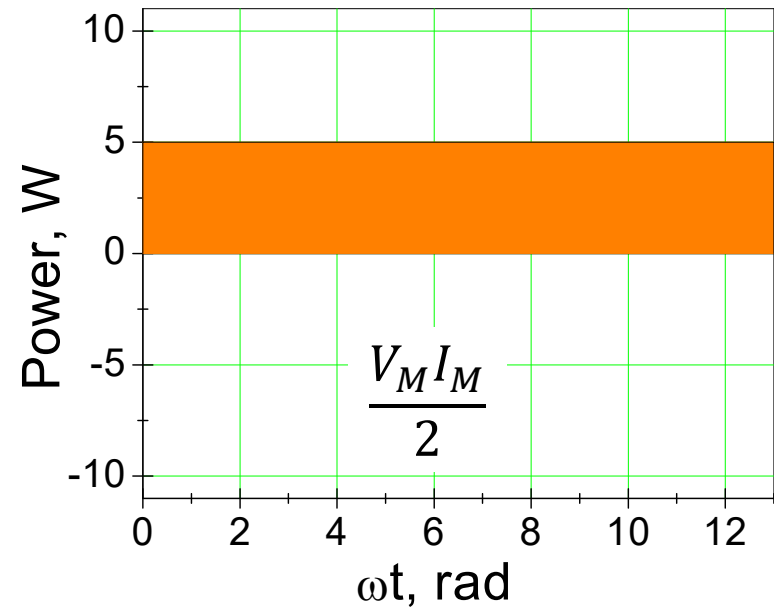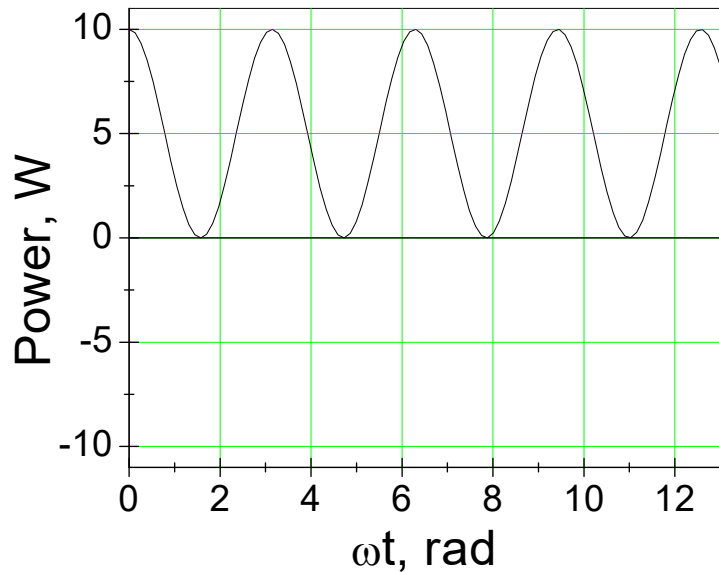
Average (“rms”) power dissipated in resistor



$$p(t) = v(t) \times i(t) = V_M I_M \cos^2(\omega t)$$

$$\cos^2(\omega t) = (1/2) [1 + \cos(2\omega t)]$$
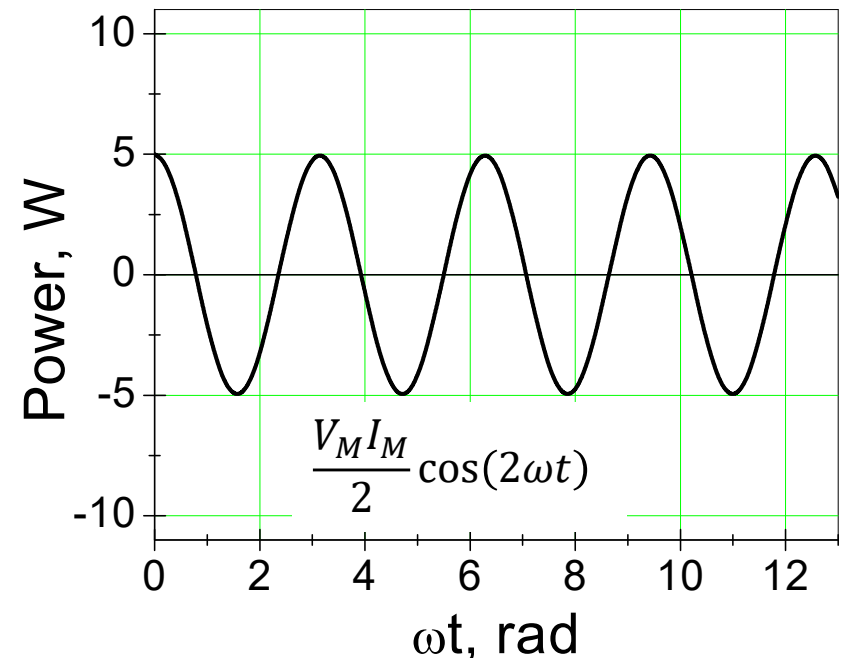
$$p(t) = \frac{V_M I_M}{2} + \frac{V_M I_M}{2} \cos(2\omega t)$$




$$P_{\text{rms}} = V_M I_M / 2$$

$$V_{\text{eff}} = V_M / \sqrt{2}$$

$$I_{\text{eff}} = I_M / \sqrt{2}$$

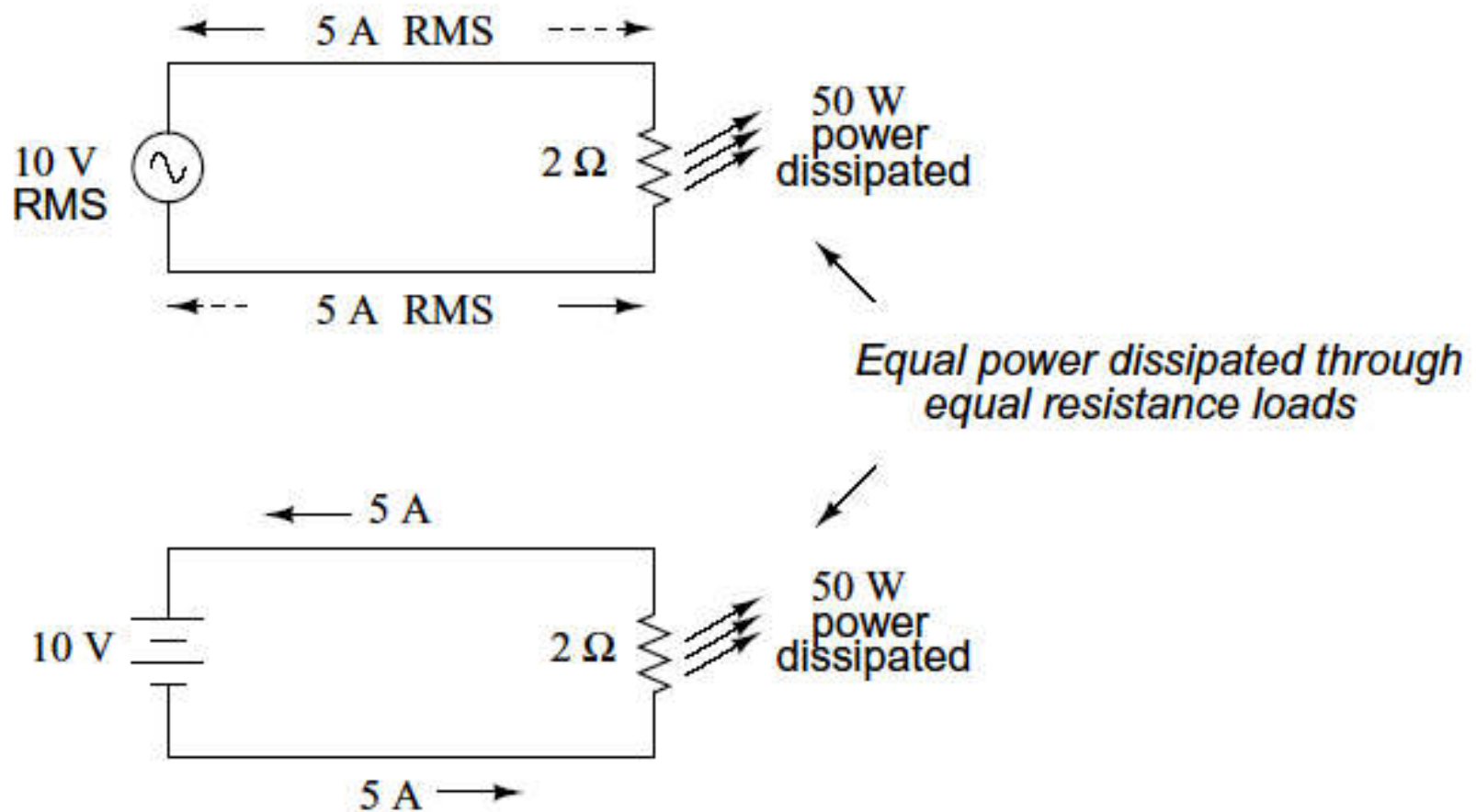
Average (RMS) characteristics of sine waves



The sine voltage source with the effective (rms) voltage 10V produces the same power as the DC battery with 10 V voltage

The equivalent DC voltage (producing the same Joule heat as the AC voltage) is called ***RMS voltage (Root Mean Square) or effective value***

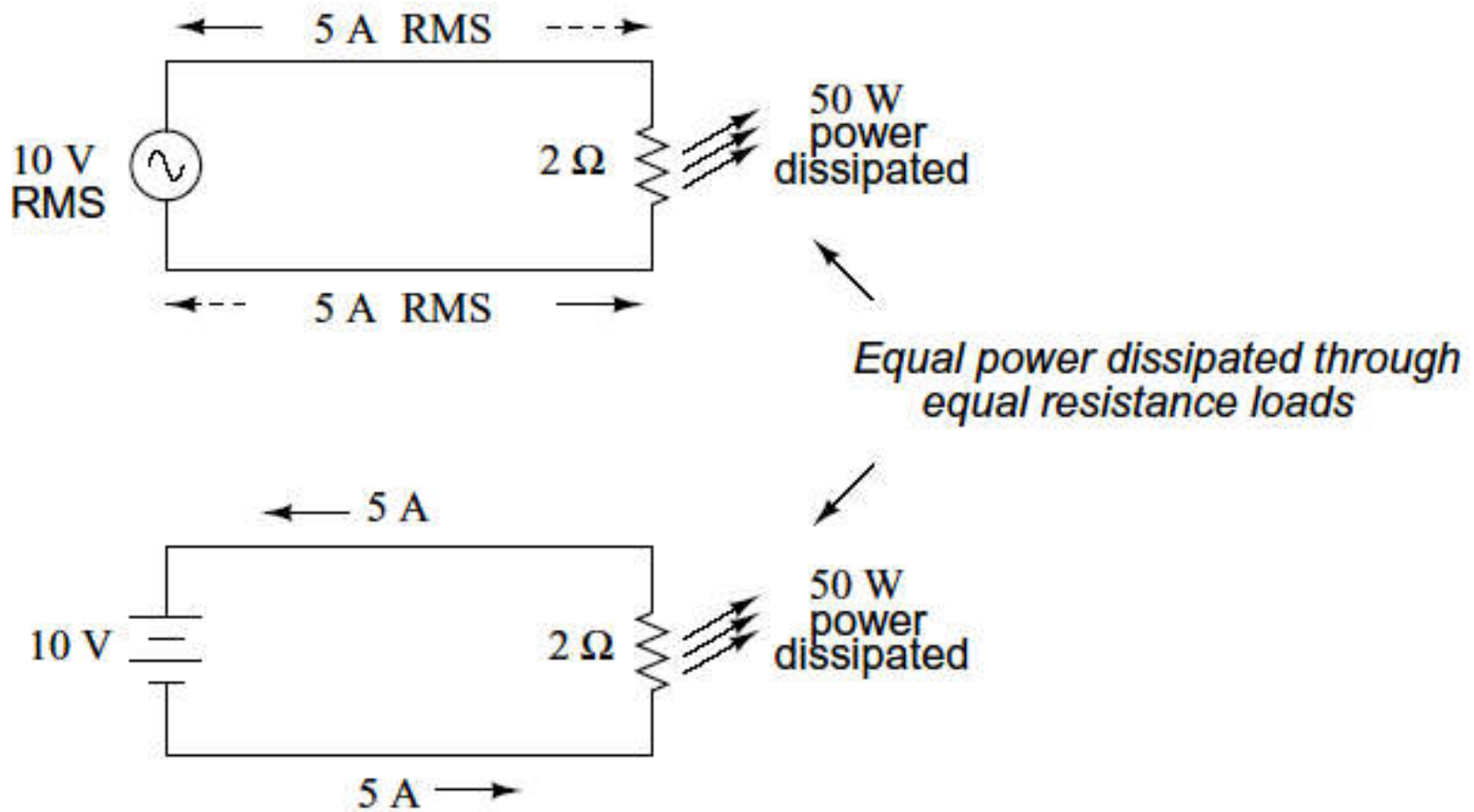Average (RMS) characteristics of sine waves



$$V_{RMS} = V_M / \sqrt{2} = 0.707 V_M$$

What is the amplitude of the AC source above?

$$V_M = V_{RMS} / 0.707 = 10V / 0.707 = 14.14 V$$

AC powers in R-L-C circuits

There is a phase angle between the current and voltage:

$$i = I_M \cos(\omega t); v = V_M \cos(\omega t + \varphi);$$

The instantaneous power:

$$p(t) = v(t) \times i(t) = V_M \cos(\omega t + \varphi) \times I_M \cos(\omega t) = \\ V_M I_M \cos(\omega t + \varphi) \cos(\omega t)$$

$$\cos(a) \cos(b) = (1/2) [\cos(a+b) + \cos(a-b)]$$

$$a = \omega t + \varphi; b = \omega t;$$

$$\cos(a+b) = \cos(a) \cos(b) - \sin(a) \sin(b)$$

$$a = \omega t + \varphi; b = \omega t;$$

$$p(t) = \frac{V_M I_M}{2} \cos(\varphi) + \frac{V_M I_M}{2} \cos(2\omega t + \varphi)$$

$$\cos(2\omega t + \varphi) = \\ \cos(2\omega t) \cos(\varphi) - \sin(2\omega t) \sin(\varphi)$$

$$p(t) = \frac{V_M I_M}{2} \cos(\varphi) \cdot [1 + \cos(2\omega t)] - \frac{V_M I_M}{2} \sin(\varphi) \sin(2\omega t)$$

AC powers in R-L-C circuits

In R-L-C circuits, the current and voltage may **both** have a phase angle with respect to the source signal:

$$i = I_M \cos(\omega t + \varphi_i); v = V_M \cos(\omega t + \varphi_v);$$

We can offset the origin of the current and voltage waveforms by φ_i :

$$i = I_M \cos(\omega t); v = V_M \cos(\omega t + \varphi_v - \varphi_i) = V_M \cos(\omega t + \varphi);$$



where $\varphi_{vi} = \varphi_v - \varphi_i$; we can now use the previous expressions derived for $\varphi_i = 0$

$$p(t) = \frac{V_M I_M}{2} \cos(\varphi_{vi}) \cdot [1 + \cos(2\omega t)] - \frac{V_M I_M}{2} \sin(\varphi_{vi}) \sin(2\omega t)$$

where $\varphi_{vi} = \varphi_v - \varphi_i$ is the phase shift between the voltage and the current

Active (average) and reactive powers in R-L-C circuits
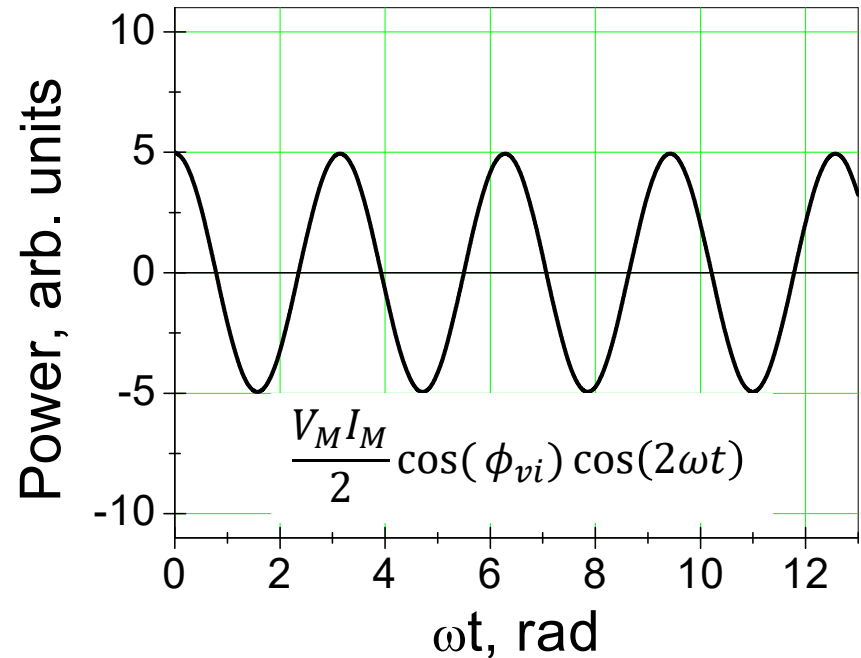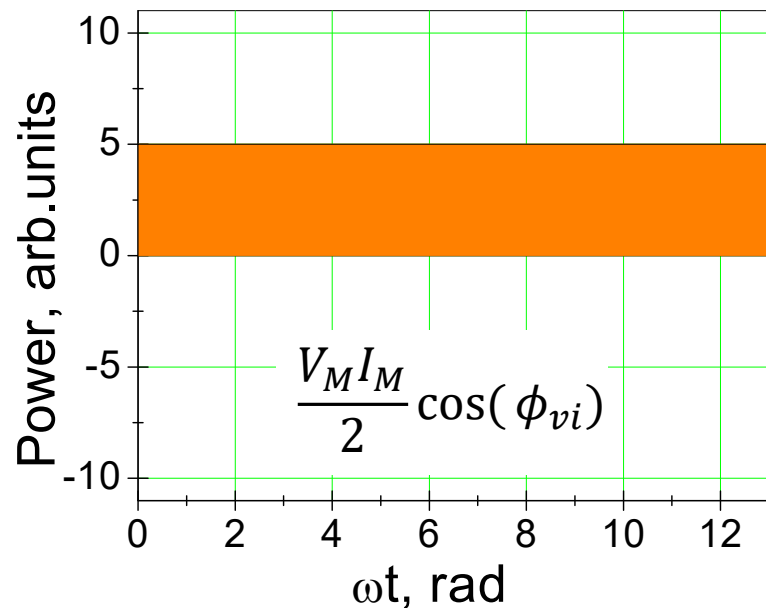
$$p(t) = \frac{V_M I_M}{2} \cos(\phi_{vi}) \cdot [1 + \cos(2\omega t)] - \frac{V_M I_M}{2} \sin(\phi_{vi}) \sin(2\omega t)$$




Active (average) power:

$$P = \frac{V_M I_M}{2} \cos(\phi_{vi}) = V_{eff} I_{eff} \cos(\phi_{vi})$$

where $\phi_{vi} = \phi_v - \phi_i$
 is the phase shift
 between the voltage and
 the current

Active (average) and reactive powers in R-L-C circuits
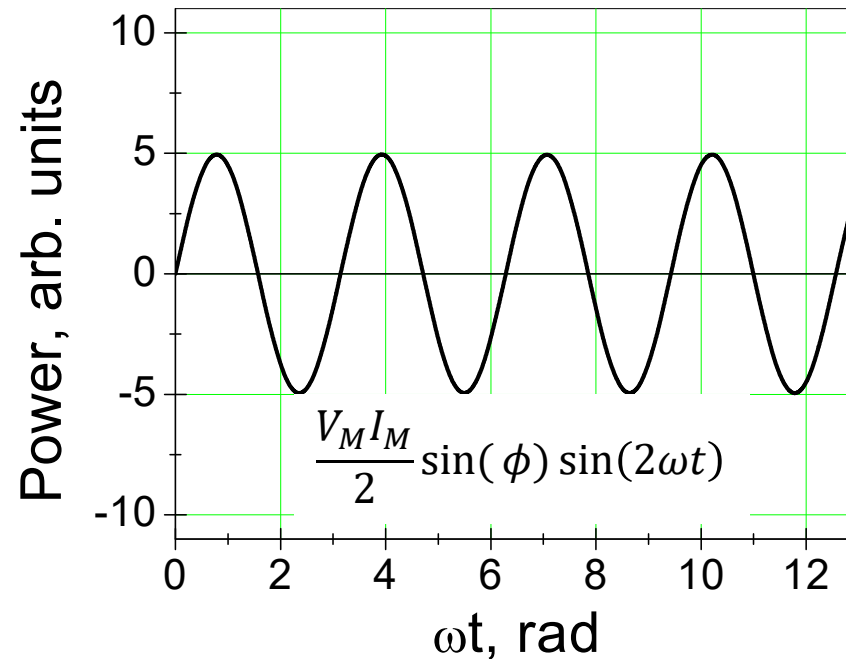
$$p(t) = \frac{V_M I_M}{2} \cos(\phi_{vi}) \cdot [1 + \cos(2\omega t)] - \frac{V_M I_M}{2} \sin(\phi_{vi}) \sin(2\omega t)$$



Reactive power:

$$Q = \frac{V_M I_M}{2} \sin(\phi_{vi}) = V_{eff} I_{eff} \sin(\phi_{vi})$$

where $\phi_{vi} = \phi_v - \phi_i$

Active (average) and reactive powers in R-L-C circuits

$$p(t) = P \cdot [1 + \cos(2\omega t)] - Q \sin(\phi_{vi}) \sin(2\omega t)$$

$$P = \frac{V_M I_M}{2} \cos(\phi_{vi})$$

$$Q = \frac{V_M I_M}{2} \sin(\phi_{vi})$$

Examples:

1. Resistive circuit: $\phi_{vi} = 0$;

$$P = V_M I_M / 2; Q = 0;$$

2. Inductance: $\phi_{vi} = -\pi/2$;

$$P = 0; Q = -V_M I_M / 2;$$

2. Capacitance: $\phi_{vi} = \pi/2$;

$$P = 0; Q = +V_M I_M / 2;$$

Complex power, active (average) and reactive powers

Given the complex voltage and current amplitudes $\hat{V}_M = V_M e^{j\phi_v}$ $\hat{I}_M = I_M e^{j\phi_i}$

We define the Complex Power as $S = \frac{\hat{V}_M \cdot \hat{I}_M^*}{2} = \frac{V_M I_M}{2} e^{j(\phi_v - \phi_i)}$ “ * ” is “complex conjugate”,

Rewriting S using Euler's formula:

$$S = \frac{V_M I_M}{2} e^{j(\phi_v - \phi_i)} = \frac{V_M I_M}{2} \cos(\phi_{vi}) + j \frac{V_M I_M}{2} \sin(\phi_{vi})$$

Where we defined $\phi_{vi} = \phi_v - \phi_i$

Hence, real part of S = active power P

And imaginary part of S = reactive power Q

Complex power S using effective (rms) values

$$\hat{V}_{eff} = \hat{V}_M / \sqrt{2}; \hat{I}_{eff} = \hat{I}_M / \sqrt{2}$$

$$S = \hat{V}_{eff} \cdot \hat{I}_{eff}^*$$

Complex power, active (average) and reactive powers

In summary (formulae in red show MATLAB functions):

*Complex power: $S = V_M * I_M^* / 2 = V_M * conj(I_M) / 2$*

Active (Average) power: $P = Re(S) = real(S)$


Reactive power, absolute value: $Q = |Im(S)| = abs(imag(S))$

Additional power characteristics (less common):

Apparent Power $|S| = abs(S) = V_M I_M / 2$

Power factor = $P / |S| = cos(\varphi_{vi})$

Example 1

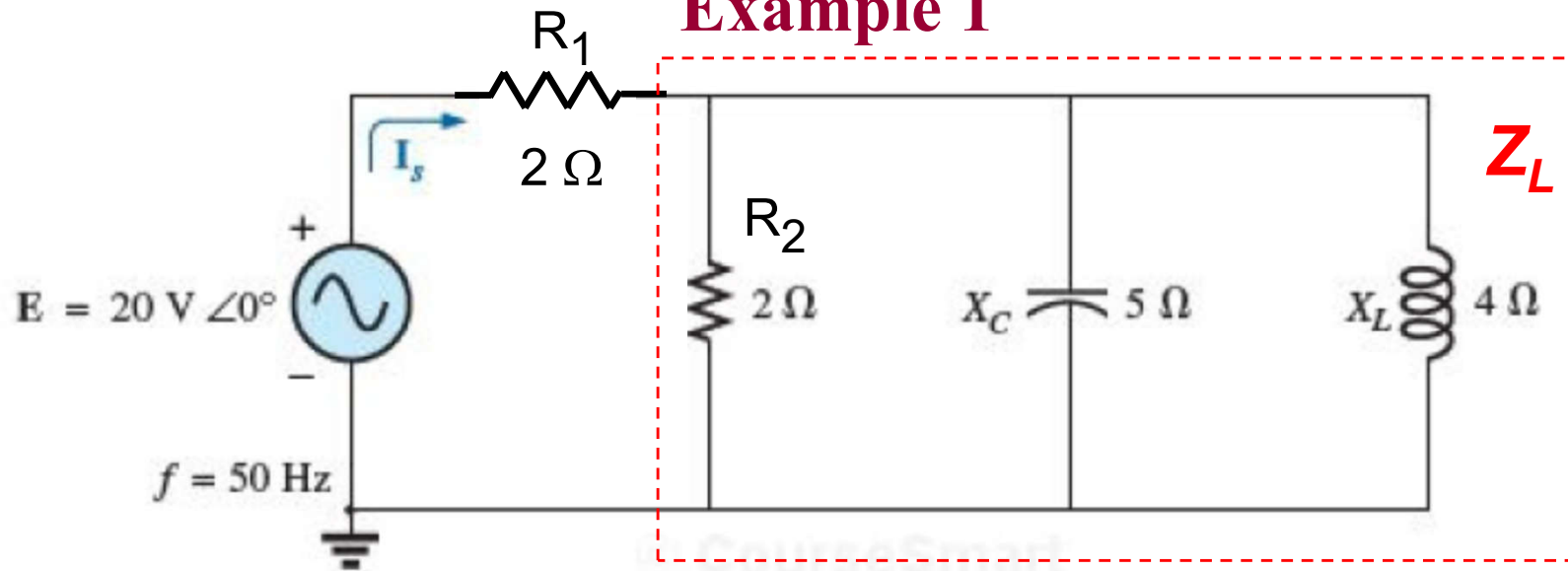

- (1) Find the average power P and reactive power Q delivered to elements R_1 , R_2 , C and L ;
- (2) Consider the R_2 - C - L combination as a load for the circuit and find the active and reactive power delivered to the load.

MATLAB code for the Example 1

```
clc
clear all
E=20;
R1=2; R2=2;
XL=4;XC=5;
ZL=j*XL;ZC=-j*XC;
%nodal analysis
Y=[1/R1+1/R2+1/ZL+1/ZC];
Is=[E/R1];
F=Y\Is;
%Voltage across R1
VR1=E-F;
%Current through R1
IR1=VR1/R1;
%Power in R1
SR1=VR1*conj(IR1)/2;
PR1=real(SR1)
QR1=imag(SR1)
```

```
%Powers in R2,C and L
%Voltage across R2,C,L = F
IR2=F/R2;
IC=F/ZC;
IL=F/ZL;
SR2=F*conj(IR2)/2;
PR2=real(SR2)
QR2=imag(SR2)
SC=F*conj(IC)/2;
PC=real(SC)
QC=imag(SC)
SL=F*conj(IL)/2;
PL=real(SL)
QL=imag(SL)
%Power in the load ZL
%Voltage across ZL = F
ZL=1/(1/R2+1/ZC+1/ZL);
IZL=F/ZL;
SZL=F*conj(IZL)/2;
PZL=real(SZL)
QZL=imag(SZL)
```

Continued in the
right column

Solution results:

PR1 = 25.1870

QR1 = 0

PR2 = 24.9377

QR2 = 0

PC = 0

QC = -9.9751

PL = 0


QL = 12.4688

PZL = 24.9377

QZL = 2.493

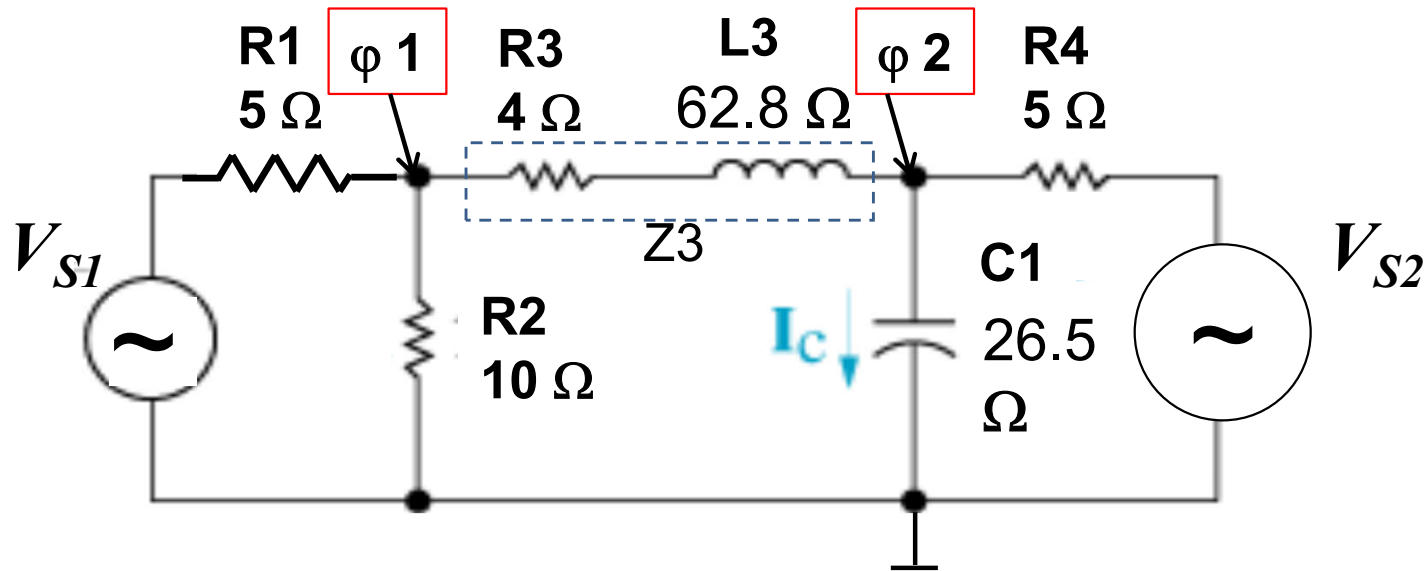Example 2 (Lecture 11: AC nodal analysis)

Find the power dissipated in component Z3



$$V_{S1}(t) = 7.5 \cos(\omega t) \text{ V} \quad \Rightarrow \quad V_{S1} = 7.5$$

$$v_{S2}(t) = 20 \cos(\omega t - 0.7 \text{ rad}) \text{ V} \quad \Rightarrow \quad V_{S2} = 20 e^{j-0.7} = 20 \angle(-0.7)$$

$$\begin{aligned} Z_{L3} &= iX_{L3}; \\ Z3 &= R3 + Z_{L3}; \\ Z_{C1} &= -iX_{C1}; \end{aligned}$$

$$Y = \begin{bmatrix} 1/R_1 + 1/R_2 + 1/Z_3 & -1/Z_3 \\ -1/Z_3 & 1/Z_3 + 1/Z_{C1} + 1/R_4 \end{bmatrix}; \quad I_S = \begin{bmatrix} V_{S1}/R_1 \\ V_{S2}/R_4 \end{bmatrix};$$

$$[\varphi] = Y^{-1} \times I_S = Y \setminus I_S; \quad I_C = \varphi(2) / Z_{C1}$$

```

clear all
clc
% <<< AC Nodal analysis >>>
%Lect 17 Ex 1
%input data
Vs1m=7.5;
Vs2m=20; Vs2ph=-0.7;
R1=5;R2=10;R3=4;R4=5;
XL3=62.8; XC1=26.5;
%Complex amplitudes and impedances
Vs1=Vs1m; %complex amplitude of Vs1(t)
Vs2=Vs2m*exp(j*Vs2ph);
ZL3=j*XL3;
ZC1=-j*XC1;
Z3=R3+ZL3;
%Y and Is matrices
Y=[1/R1+1/R2+1/Z3,-1/Z3;...
-1/Z3,1/Z3+1/ZC1+1/R4];
Is=[Vs1/R1;Vs2/R4];
Phi=Y\Is;

```

```

V3=Phi(1)-Phi(2);
I3=V3/Z3;
% <<< Power calculations >>>
S=V3*conj(I3)/2;
P=real(S) % active power in Z3
Q=abs(imag(S)) % abs. value of
% reactive power in Z3

```

Matlab output:


```

P =
    0.1443
Q =
    2.2654

```

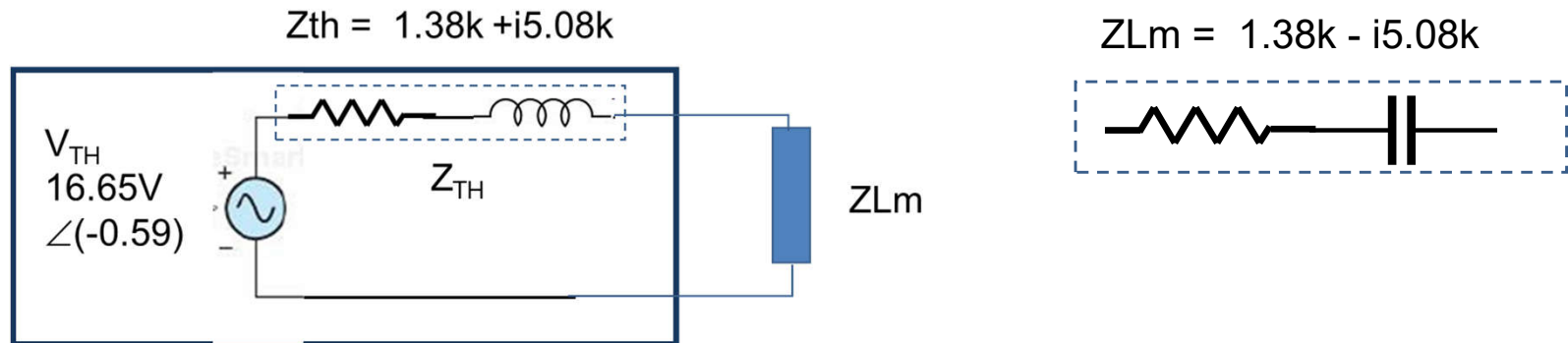Example 3

Find the active and reactive power dissipated in matching load



clear all

clc

%AC Power in the matching load

%input data

Vthm=16.65; Vthph=-0.59;

Vth=Vthm*exp(i*Vthph);

Zth=1.38e3+5.08e3i;

ZLd=conj(Zth);

ILd=Vth/(Zth+ZLd);

VLd=ILd*ZLd;

S=VLd*conj(ILd)/2;

PLd=real(S);

QLd=abs(imag(S));

disp(['Active power in the load: PL= ',num2str(PLd), ' W'])

disp(['Reactive power in the load: QL= ',num2str(QLd), ' W'])

MATLAB output for this part

Active power in the load: PLd= 0.025111 W

Reactive power in the load: QLd= 0.092437 W

Example 3 (cont)

**Find the physical equivalent circuit of the matching load;
assume that $f=2\text{MHz}$**

MATLAB code (continued from the previous slide):

```
%Equivalent circuit of the matching load at 2 MHz
f=2e6; om=2*pi*f;
%Resistance of matching load
RLd=real(ZLd);
disp(['Matching load contains resistance RLd= ',...
num2str(RLd),' Ohm in series with'])
% The sign of imag(ZLd)
ImZLd=imag(ZLd);
if ImZLd>0, %load contains inductor
XLLd=ImZLd; %equivalent inductor reactance XLd=om*LLd
LLd=XLLd/om;
disp(['inductor LLd= ', num2str(LLd),' H'])
else %load contains capacitor
XCLd=-ImZLd; %capacitor reactance XCLd=1/(om*CLd)
CLd=1/(om*XCLd);
disp(['capacitor CLd= ', num2str(CLd),' F'])
end
```

Output for this part

Matching load contains
resistance RLd= 1380 Ohm
in series with
capacitor CLd= 1.5665e-11 F